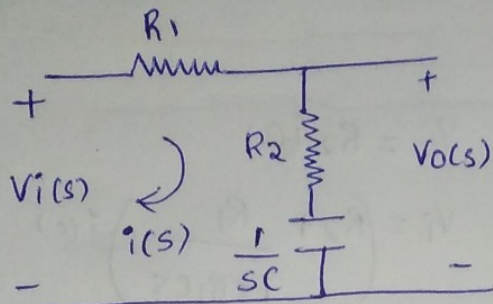


CS LAB (lab-0)

511824

1) Design and study of lag, lead, laglead compensators.

a) Lag compensator:-



$$V_o(s) = \left(R_2 + \frac{1}{sC} \right) i(s)$$

$$V_i(s) = \left(R_1 + R_2 + \frac{1}{sC} \right) i(s)$$

⇒ Transfer function;

$$\frac{V_o(s)}{V_i(s)} = \frac{R_2 + \frac{1}{sC}}{R_1 + R_2 + \frac{1}{sC}}$$


$$= \frac{sR_2C + 1}{s(R_1 + R_2)C + 1}$$

$$= \left(\frac{s + \frac{1}{R_2C}}{s + \frac{1}{(R_1 + R_2)C}} \right) \frac{R_1 + R_2}{R_2}$$

Let $K = \frac{R_1 + R_2}{R_2}$; $T = R_2C$

$$\Rightarrow \frac{V_o}{V_i} = \left(\frac{s + \frac{1}{T}}{s + \frac{1}{KT}} \right) \cdot \frac{1}{K}$$

pole zero plot:

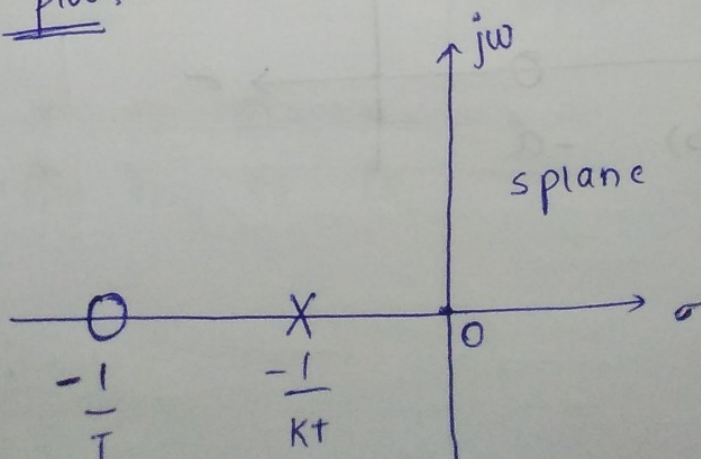


$$K = \frac{R_1 + R_2}{R_2} = 1 + \frac{R_1}{R_2} (> 1)$$

$$\Rightarrow \frac{1}{T} > \frac{1}{KT}$$

1)

b) lead compensator:

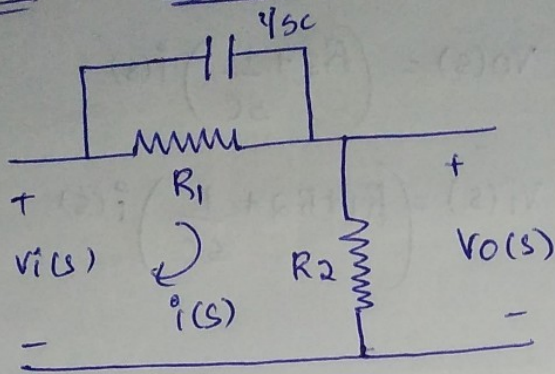

$$V_o = R_2 i(s)$$

$$V_i = \left(R_2 + \frac{R_1}{1 + R_1 C s} \right) i(s)$$

$$\Rightarrow \frac{V_o(s)}{V_i(s)} = \frac{R_2}{R_2 + \frac{R_1}{1 + R_1 C s}}$$

$$= \frac{R_2 (1 + R_1 C s)}{R_2 (1 + R_1 C s) + R_1}$$


$$= \frac{R_1 R_2 C \left[s + \frac{1}{R_1 C} \right]}{R_1 R_2 C \left[s + \frac{1}{R_1 C} + \frac{1}{R_2 C} \right]}$$

$$= \frac{s + a}{s + a + b}$$


$$a = \frac{1}{R_1 C}$$

$$b = \frac{1}{R_2 C}$$

pole-zero plot:

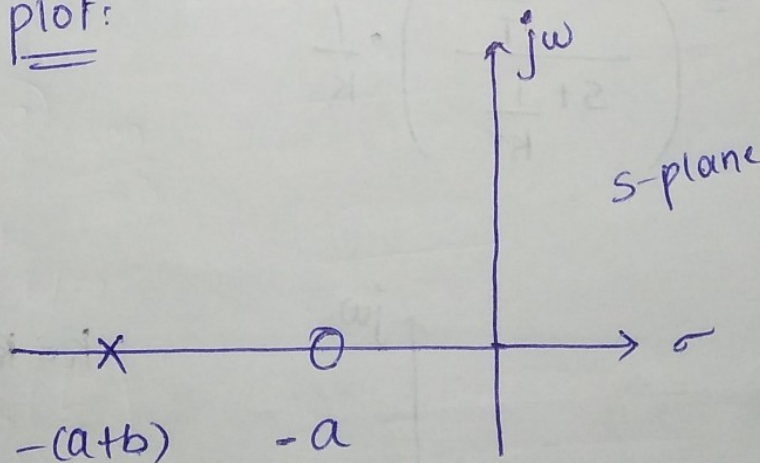

c) lag-lead compensator:

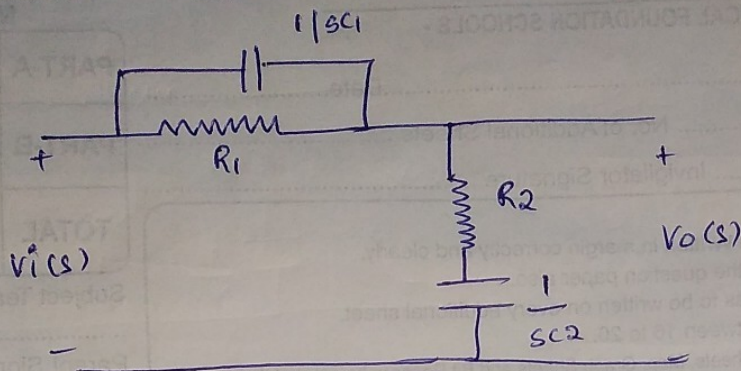


$$\begin{aligned} \frac{V_o(s)}{V_i(s)} &= \frac{R_2 + \frac{1}{sC_2}}{R_2 + \frac{1}{sC_2} + \frac{R_1}{1+sR_1C_1}} \\ &= \frac{(sR_2C_2 + 1) \cdot (sR_1C_1 + 1)}{sR_2C_2 + s^2 R_1 R_2 C_1 C_2 + sR_1C_2 + sR_1C_1 + 1} \\ &= \frac{(sR_2C_2 + 1)(sR_1C_1 + 1)}{s^2 R_1 R_2 C_1 C_2 + s(R_1C_1 + R_2C_2 + R_1C_2) + 1} \end{aligned}$$

\Rightarrow 2 poles 2 zeroes

Let $z_1, z_2 \rightarrow$ zeroes
 $p_1, p_2 \rightarrow$ poles

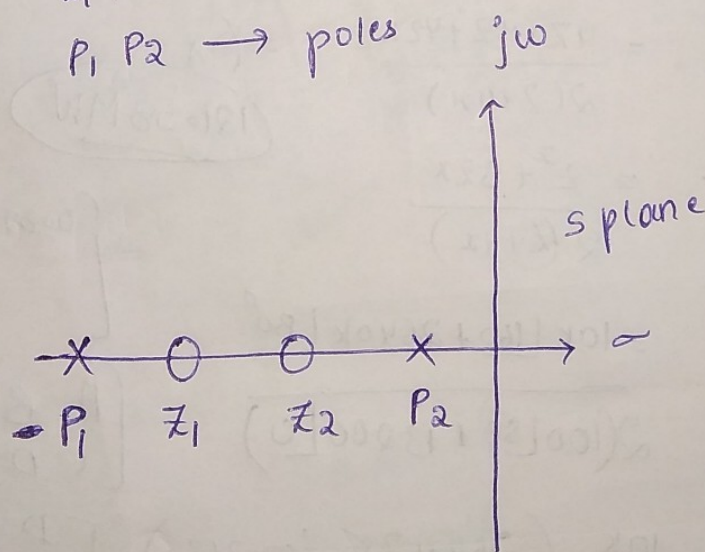combination of both lag
and lead compensators



$$z_1 = -\frac{1}{R_1 C_1}$$


$$z_2 = -\frac{1}{R_2 C_2}$$

~~P1, P2~~

$$\Rightarrow \frac{V_o(s)}{V_i(s)} = \frac{\left(s + \frac{1}{R_1 C_1}\right) \left(s + \frac{1}{R_2 C_2}\right)}{s^2 + s \left(\frac{R_1 C_1 + R_2 C_2 + R_1 C_2}{R_1 R_2 C_1 C_2}\right) + \frac{1}{R_1 R_2 C_1 C_2}}$$

i)

d) P-controller:

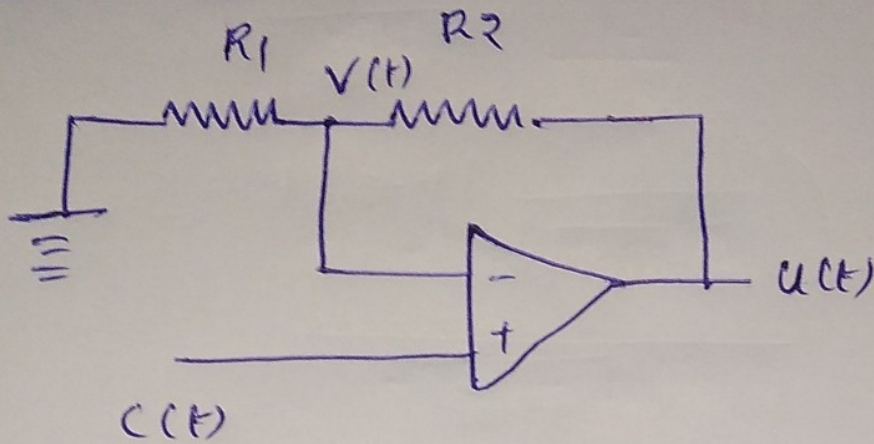

By virtual ground concept

$$V(t) = C(t) \Rightarrow V(s) = C(s)$$


$$\Rightarrow \frac{C(s)}{R_1} + \frac{C(s) - U(s)}{R_2} = 0$$

$$\Rightarrow C(s) \left[\frac{1}{R_1} + \frac{1}{R_2} \right] = \frac{U(s)}{R_2}$$

$$\Rightarrow \frac{U(s)}{\cancel{R_2}} = \frac{C(s) [R_1 + R_2]}{R_1 \cancel{R_2}}$$

$$\frac{U(s)}{C(s)} = \frac{R_1 + R_2}{R_1} = \text{constant value.}$$

PD-controller:

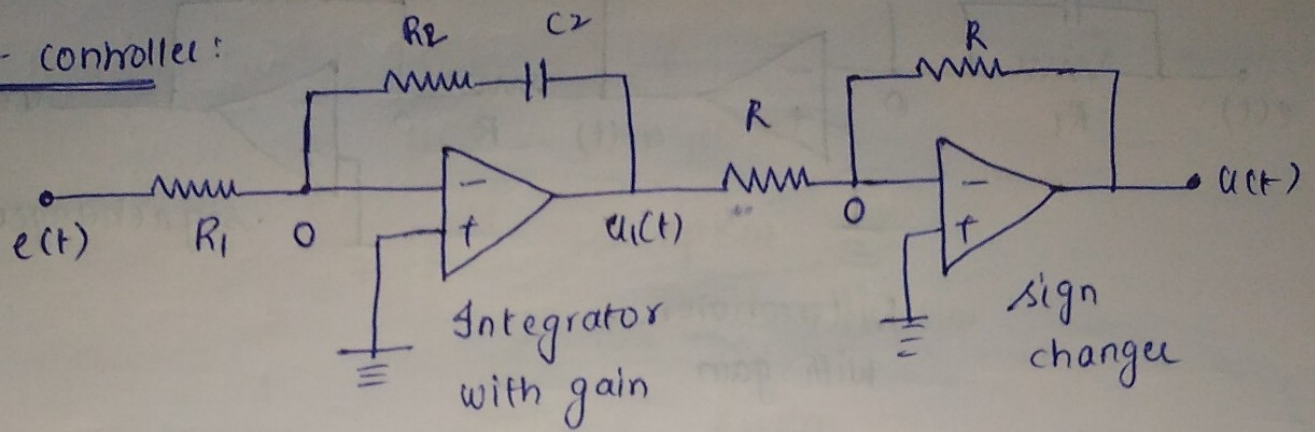

$$-\frac{e(s)}{R_1} + \frac{(-u_1(s))}{R_2 + \frac{1}{Cs}} = 0 \Rightarrow \frac{e_1(s)}{R_1} = \frac{-u_1(s) \cdot Cs}{SR_2Cs + 1} \rightarrow \textcircled{1}$$

$$\frac{0 - u_1(s)}{R} + \frac{0 - u(s)}{R} = 0 \Rightarrow u_1(s) = -u(s) \rightarrow \textcircled{2}$$

$$\Rightarrow \frac{e_1(s)}{R_1} = \frac{-u_1(s) \cdot Cs}{SR_2Cs + 1}$$


$$= \frac{u(s) \cdot Cs}{SR_2Cs + 1}$$

$$\Rightarrow \frac{e_1(s)}{u(s)} = \frac{SR_1C_2}{SR_2Cs + 1}$$

$$\text{Transfer fun}^n = \frac{u(s)}{e(s)} = \frac{SR_2Cs + 1}{SR_1C_2} = \frac{\left(s + \frac{1}{R_2C_2}\right) R_2C_2}{SR_1C_2}$$

$$= \frac{R_2}{R_1} \left(\frac{s + \frac{1}{R_2C_2}}{s} \right)$$


Pole-zero plots:

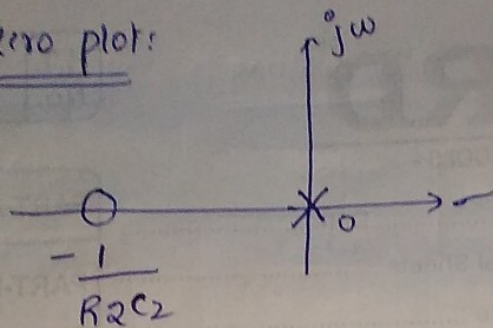

1)

f)

PD-controller:

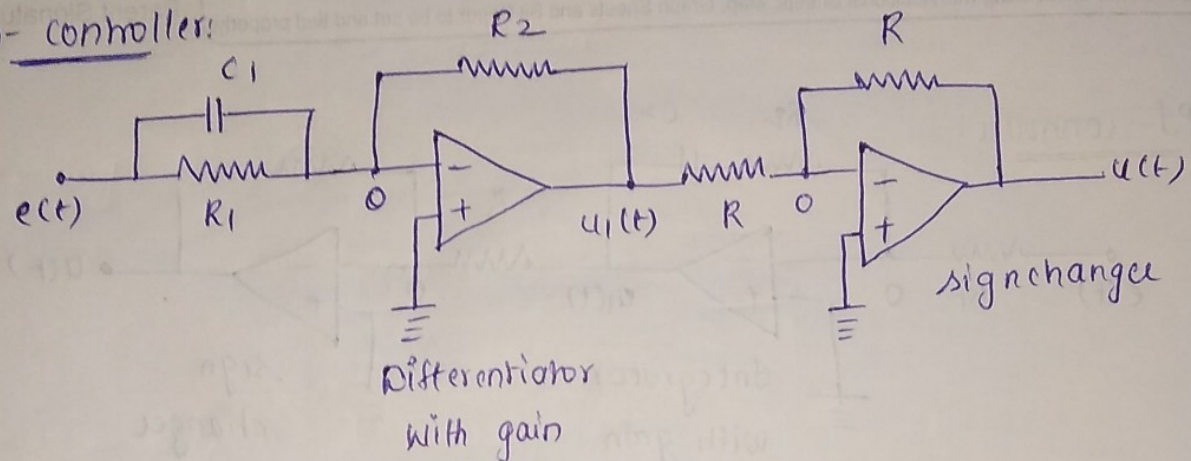


$$\frac{0 - u_1(s)}{R} + \frac{0 - u(s)}{R} = 0 \Rightarrow u_1(s) = -u(s) \rightarrow \textcircled{1}$$

$$\frac{0 - e(s)}{\left(\frac{R_1}{1 + R_1 C_1 s}\right)} + \frac{(-u_1(s))}{R_2} = 0$$


$$\Rightarrow \frac{e(s)(1 + R_1 C_1 s)}{R_1} = -\frac{u_1(s)}{R_2} = \frac{u(s)}{R_2}$$
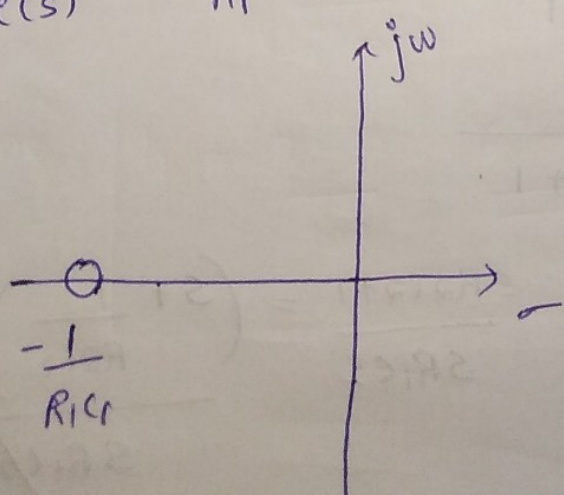
$$\Rightarrow \frac{u(s)}{e(s)} = \frac{R_2}{R_1} (1 + R_1 C_1 s) = R_2 C_1 \left[s + \frac{1}{R_1 C_1} \right]$$



1)

g) Servo motor:

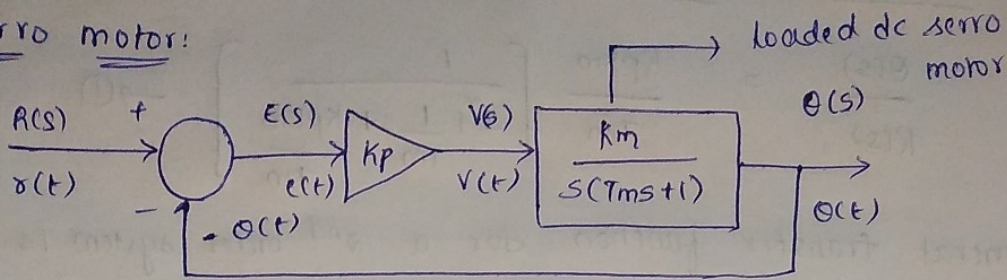

$$\text{Gain (openloop)} G = \frac{K_p K_m}{s(T_m s + 1)} ; H = 1$$


$$\begin{aligned} \text{Transfer fun}^n; \frac{\Theta(s)}{R(s)} &= \frac{G}{1 + GH} \\ &= \frac{K_p K_m}{s(T_m s + 1) + K_p K_m} \\ &= \frac{K_p K_m}{s^2 T_m + s + K_p K_m} \end{aligned}$$

$$= \frac{K_p K_m}{T_m} \left[\frac{1}{s^2 + \frac{1}{T_m} s + \frac{K_p K_m}{T_m}} \right]$$

$$s = \frac{-1}{T_m} \pm \sqrt{\frac{1}{T_m^2} - \frac{4K_p K_m}{T_m}}$$

$$\text{let } \alpha = \frac{-1 + \sqrt{1 - 4K_p T_m K_m}}{2T_m} \quad \beta = \frac{-1 - \sqrt{1 - 4K_p T_m K_m}}{2T_m}$$

poles $\rightarrow \alpha, \beta$

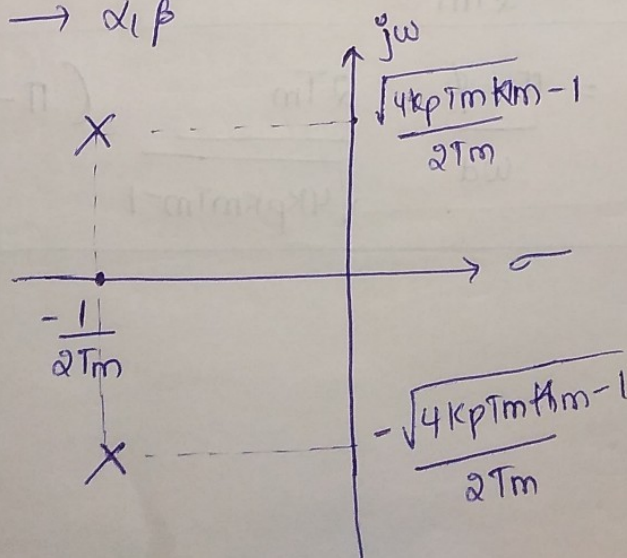

$$\alpha = \frac{-1}{2T_m} + j \left[\frac{\sqrt{4K_p T_m K_m - 1}}{2T_m} \right]$$

$$\beta = \frac{-1}{2T_m} - j \left[\frac{\sqrt{4K_p T_m K_m - 1}}{2T_m} \right]$$

b)

Time domain specifications:

$$\frac{O(s)}{R(s)} = \frac{K_p K_m}{T_m} \left[\frac{1}{s^2 + \frac{1}{T_m} s + \frac{K_p K_m}{T_m}} \right] \rightarrow (1)$$

General transfer function for a 2nd order system is

$$\frac{O(s)}{R(s)} = \frac{\omega_n^2}{s^2 + 2\xi\omega_n s + \omega_n^2} \rightarrow (2)$$

comparing (1) & (2)

$$\omega_n^2 = \frac{K_p K_m}{T_m} \Rightarrow \omega_n = \sqrt{\frac{K_p K_m}{T_m}}$$

$$\xi\omega_n = \frac{1}{2T_m} \leftarrow 2\xi\omega_n = \frac{1}{T_m} \Rightarrow \xi = \frac{1}{T_m} = \frac{1}{2\sqrt{\frac{K_p K_m}{T_m}}} = \frac{1}{2\sqrt{K_p K_m T_m}}$$

$$\phi^0 = \tan^{-1} \left(\frac{\sqrt{1-\xi^2}}{\xi} \right) = \cos^{-1}(\xi)$$

$$\phi^c = \frac{\pi}{180} \cos^{-1}(\xi)$$

$$\omega_d = \omega_n \sqrt{1-\xi^2} = \sqrt{\frac{K_p K_m}{T_m}} \cdot \frac{\sqrt{4K_p K_m T_m - 1}}{2\sqrt{T_m K_p K_m}}$$

$$= \frac{1}{2T_m} \sqrt{4K_p K_m T_m - 1}$$

$$i) \text{ rise time ; } t_r = \frac{\pi - \phi}{\omega_d} = \frac{2T_m}{\sqrt{4K_p K_m T_m - 1}} (\pi - \phi^c) \text{ (seconds)}$$

ii) delay time:

$$T_d = \frac{1 + 0.7 \xi}{\omega_n}$$

$$= \frac{1 + 0.7 \left(\frac{1}{2\sqrt{K_p K_m T_m}} \right)}{\sqrt{\frac{K_m K_p}{T_m}}}$$

$$= \sqrt{\frac{T_m}{K_m K_p}} + \frac{0.35}{\sqrt{K_m K_p}} = \frac{0.35 + \sqrt{K_m K_p T_m}}{\sqrt{K_m K_p}} \text{ sec}$$

iii) Peak time:

$$T_p = \frac{\pi}{\omega_d} = \frac{\pi}{\omega_n \sqrt{1 - \xi^2}}$$

$$= \frac{2\pi T_m}{\sqrt{4K_p K_m T_m - 1}} \text{ sec}$$

iv) Peak overshoot:

$$MP = e^{-\frac{\xi \pi}{\sqrt{1 - \xi^2}}}$$

$$= e^{-\frac{1}{2\sqrt{K_p K_m T_m}} \times \frac{\pi}{\sqrt{1 - \frac{1}{4K_p K_m T_m}}}}$$

$$= e^{-\frac{\pi}{\sqrt{4K_p K_m T_m - 1}}}$$

$$v) \text{ Settling time } = \frac{4}{\xi \omega_n} \rightarrow 2\%$$

$$= \frac{3}{\xi \omega_n} \rightarrow 5\%$$

$$\Rightarrow T_s = 8T_m \rightarrow 2\%$$

$$= 6T_m \rightarrow 5\%$$


2) Basic difference b/w 1st order & second order system.

1st order

* Only one independent energy storage element is present.

Ex: RC circuit

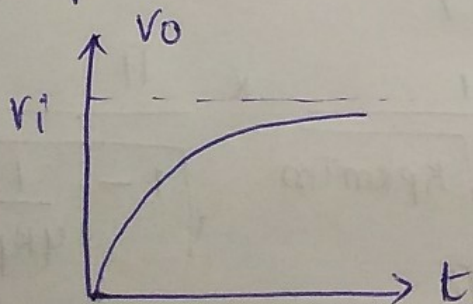* Response does not have any ripples irrespective of position of poles.



2nd order

* 2 independent energy storage elements

Ex: RLC circuit

* Exhibits oscillatory behaviour.

